

Course No: CSE 306

Assignment on 4bit ALU Design and Simulation

Section: B2

~~Group~~

Group No: 5

Student IDs: 1705096
1705095
1705097
1705102
1705104


Date of submission: 26-3-2021

Introduction:

An arithmetic logic unit is a multi-operation, combinatorial logic digital function. It can perform a set of basic arithmetic operations and a set of logic operations. The ALU has a number of selection lines to select a particular operation in the unit. The selection lines are decoded within the ALU so that k selection variables can specify up to 2^k distinct operations. Here we design a 4 bit ALU with 3 selection lines.

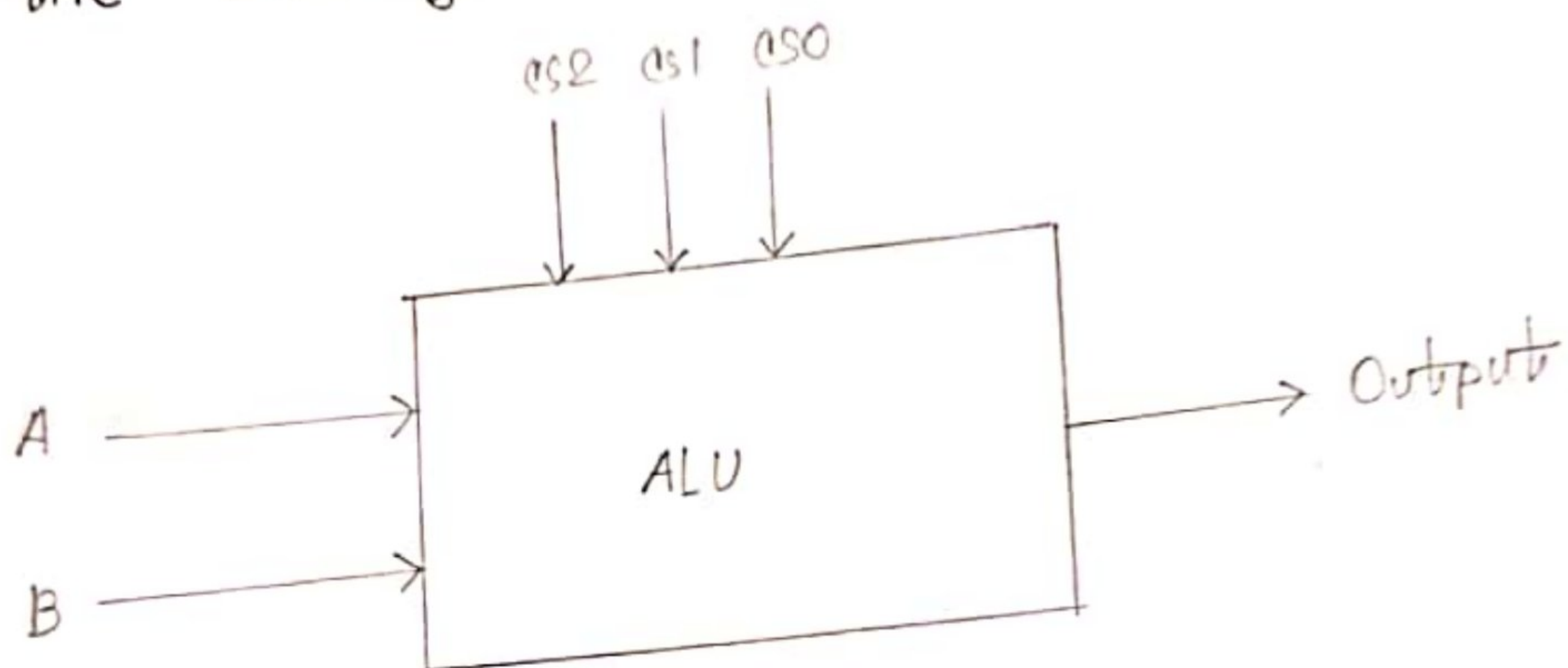Problem Specification with assigned instructions

Here we are going to design a 4 bit ALU with 3 selection variables that can simulate the following design:



cs2	cs1	cs0	Output
0	0	0	$A + B$
0	1	0	$A + B + 1$
0	x	1	$A \oplus B$
1	0	0	A
1	1	0	$A + 1$
1	x	1	AB

Truth Table & Required k-maps:

Function Table:

CS0	CS2	CS1	X_i	Y_i	Z_1	$Z_i (i \neq 1)$	Output
0	0	0	A_i	B_i	0	C_i	$A+B$
0	0	1	A_i	B_i	1	C_i	$A+B+1$
0	1	0	A_i	0	0	C_i	A
0	1	1	A_i	0	1	C_i	$A+1$
1	0	X	A_i	B_i	0	0	$A \oplus B$
1	1	X	$A_i + B_i'$	B_i'	0	0	AB

We have, $X_i = PA_i + Q(A_i + B_i') = (P+Q)A_i + QB_i'$

$$Y_i = RB_i + SB_i'$$

$$Z_i = TC_i$$

where P, Q, R, S, T is function of selectors
 for which $P=1$ when $X_i = A_i$, $Q=1$ when
 $A_i = A_i + B_i'$, $R=1$ when $Y_i = B_i$, $S=1$ when
 $Y_i = B_i'$, $T=1$ when $Z_i = C_i$

Truth Table:

$Q_2 Q_1$	Q_2	Q_1	P	Q	R	S	T	$P+Q$	Z_1
00	0	0	1	0	1	0	1	1	0
01	0	1	1	0	1	0	1	1	1
10	1	0	1	0	0	0	1	1	0
11	1	1	1	0	0	0	1	1	1
00	0	0	1	0	1	0	0	1	0
01	0	1	1	0	1	0	0	1	0
10	1	0	0	1	0	1	0	1	0
11	1	1	0	1	0	1	0	1	0

k-maps:

$Q_2 Q_1$
 Q_2 00 01 11 10
 Q_1 00 01 11 10

0	1	1	1
1	1	1	1

k-map for $P+Q$

$Q_2 Q_1$
 Q_2 00 01 11 10
 Q_1 00 01 11 10

0	0	0	0
1	0	0	1

k-map for Q

$Q_2 Q_1$
 Q_2 00 01 11 10
 Q_1 00 01 11 10

0	1	1	0
1	1	1	0

k-map for R

$Q_2 Q_1$
 Q_2 00 01 11 10
 Q_1 00 01 11 10

0	0	0	0
1	0	0	1

k-map for S

	$c s_2 c s_1$	00	01	11	10
$c s_0$	0	1	1	1	1
1		0	0	0	0

k-map for T

	$c s_2 c s_1$	00	01	11	10
$c s_0$	0	0	1	1	0
1		0	0	0	1

k-map for Z_1

Equation:

From k-maps, we have,

$$P+Q=1, Q = c s_2 c s_0, R = c s_2', S = c s_2 c s_0$$

$$T = c s_0', Z_1 = c s_1 c s_0'$$

$$\text{So that, } X_i = A_i + c s_2 c s_0 B_i', i=1,2,3,4$$

$$Y_i = c s_2' B_i + c s_2 c s_0 B_i', i=1,2,3,4$$

$$Z_i = c s_0' c_i, i=2,3,4$$

$$Z_1 = c s_1 c s_0'$$

For flags we have,


$$V = \text{cout} \oplus c_4$$

$$c = \text{cout}$$

$$S = F_4$$


$$Z = (F_1 + F_2 + F_3 + F_4)'$$

Block Diagram:

 


Block Diagram of 4 bit ALU


Circuit Diagram:

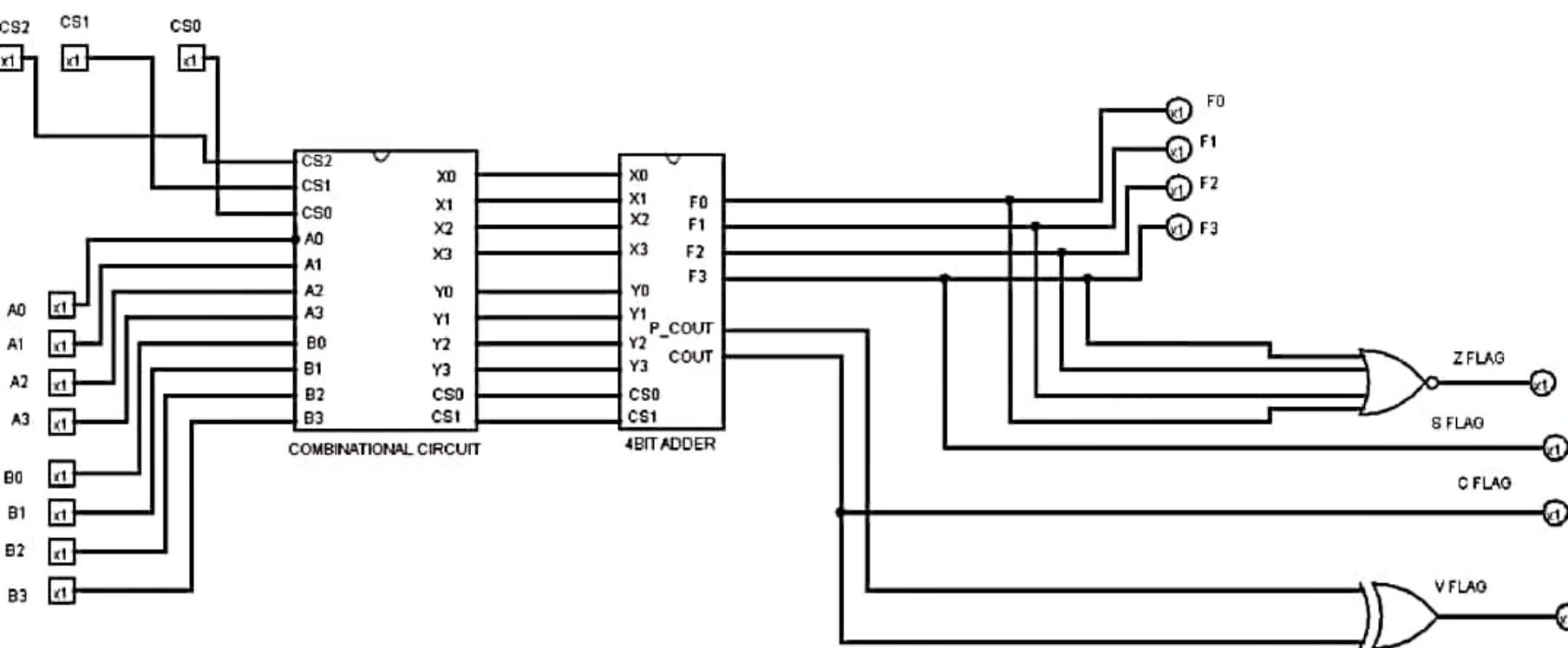


Full ALU

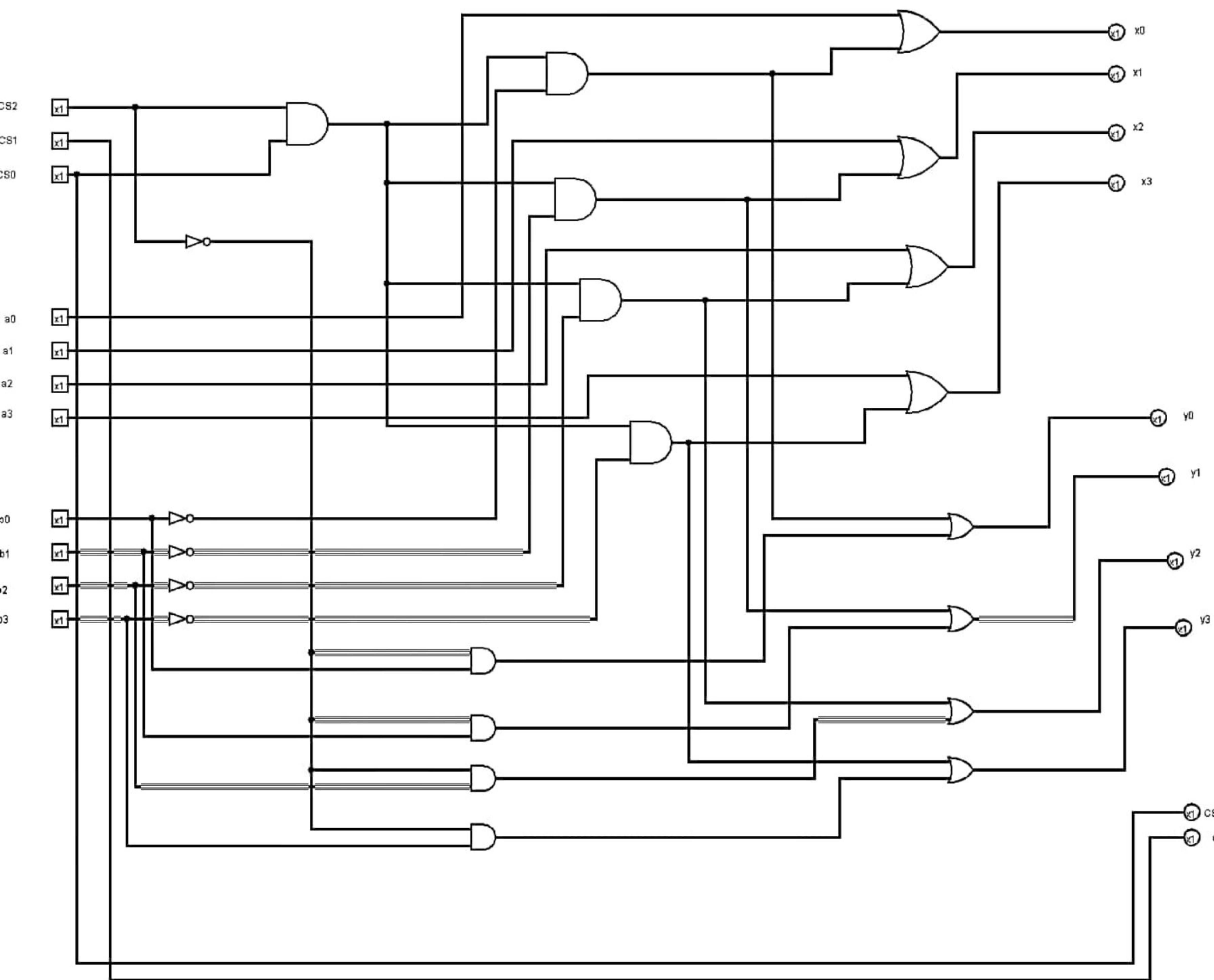


Combinational Part

 

Full Adder

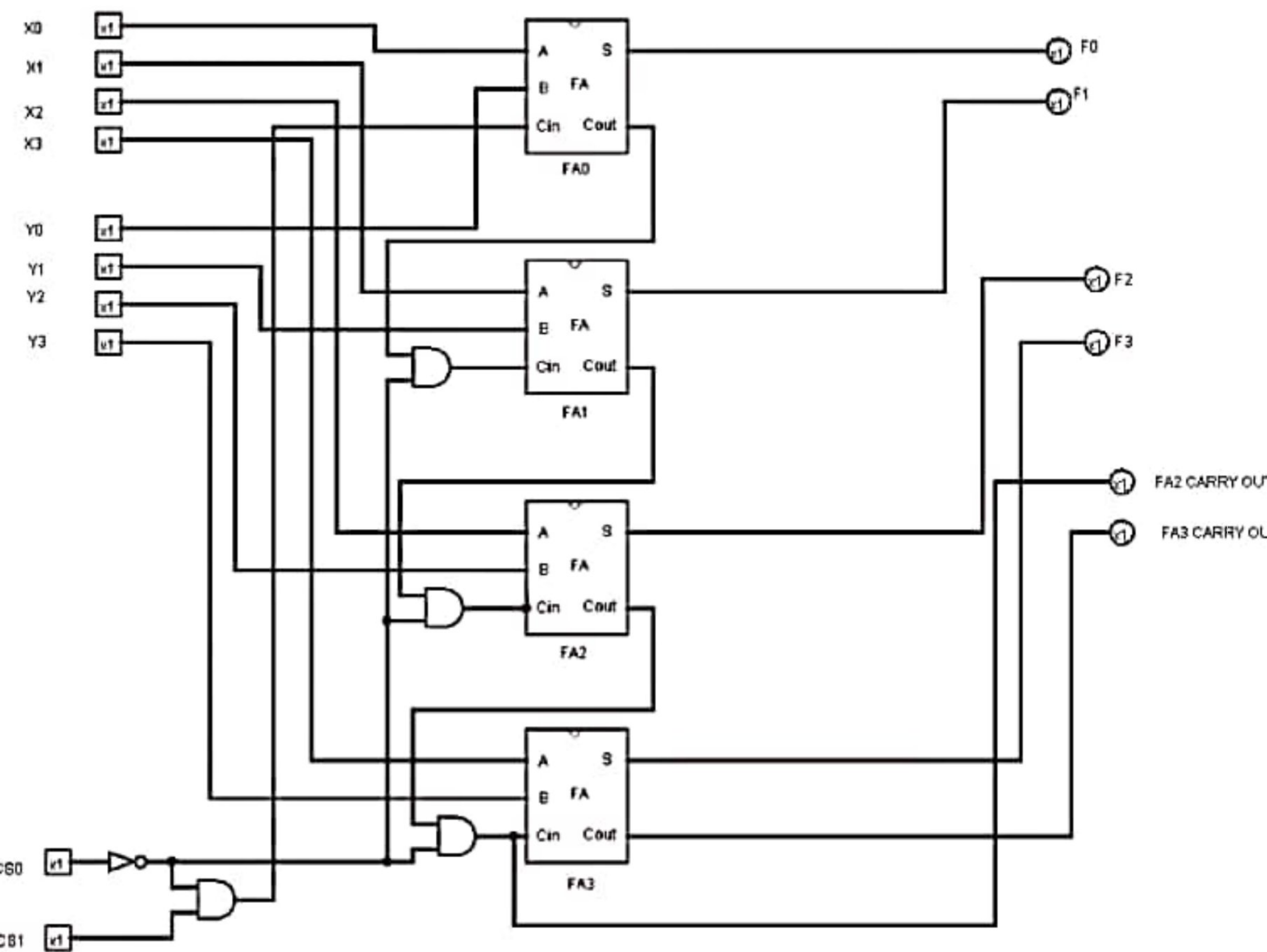

4bit Parallel Full Adder Part

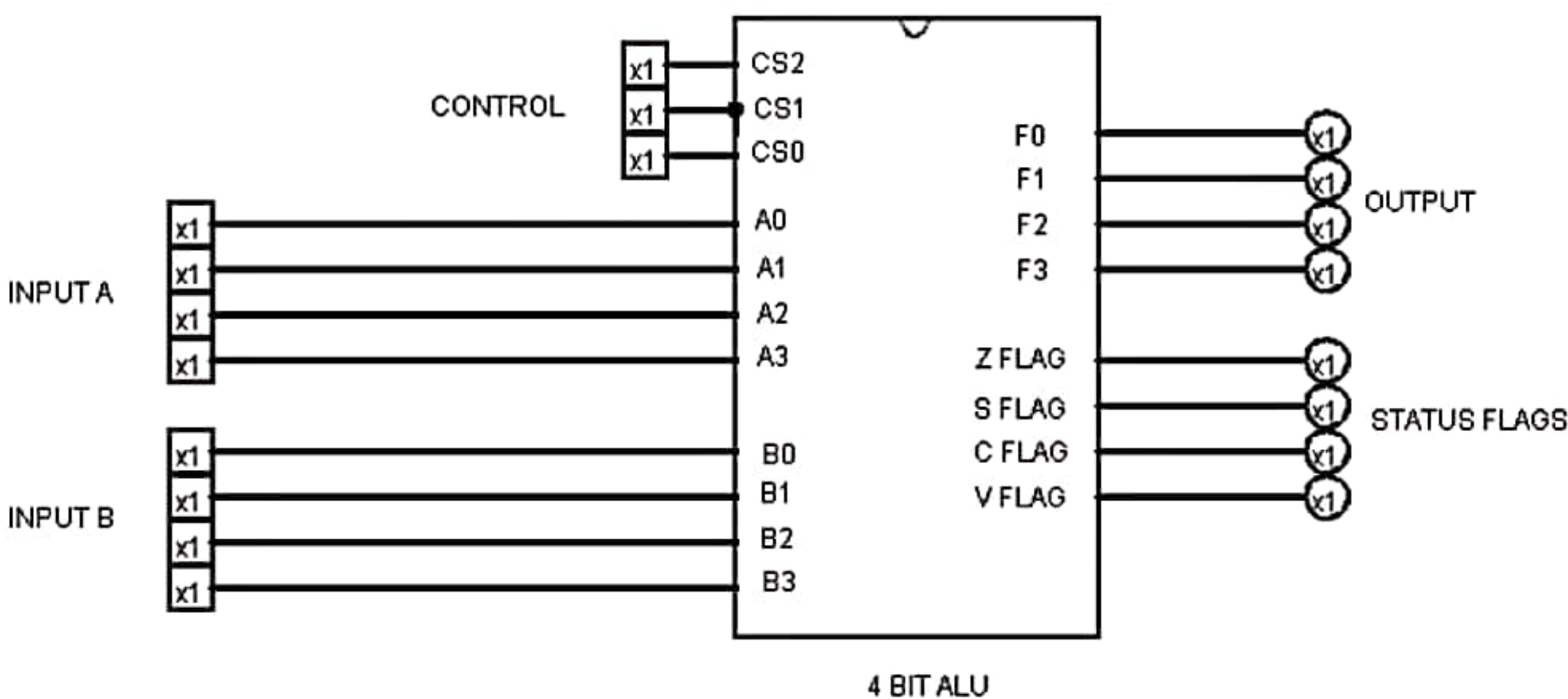

Full ALU

Ics used with count as chart:

Ic name	Ic count
7425	1
7486	3
7404	1
7408	5
7432	3

Simulator Used:

Logisim 2.7.1

Discussion:

We designed the ALU in logisim simulator. First we made a full adder using basic gates, i.e. XOR, AND and OR gates. Then we focused on the combinatorial circuit. The combinatorial circuit has three control inputs, cs_0 , cs_1 , and cs_2 which determine the operations the ALU will perform. The combinatorial circuit also has two 4 bit inputs. After making the combinatorial circuit, we made 4 bit full adder circuit using the subcircuit of the full adder we made before. This 4 bit full adder has 2, 4 bit inputs, 1 bit carry in and 1 bit carry out, and one 4 bit output.

After making all necessary sub-circuits, we made the main ALU circuit. We used the sub-circuit of the combinatorial circuit and the sub-circuit of 4-bit adder. We also implemented the flag register.